

**Bilkent University**  
**EE102-02 Lab 4 Report:**  
**Arithmetic Logic Unit**

Mehmet Emre Uncu - 22003884

**Purpose:**

This lab's goal was to create an arithmetic logic unit (ALU) using VHDL to do at least one bitwise operation and one shift operation. The mathematical functions are addition, subtraction, comparator, left logical shifter, one's complement, AND, NOR, XNOR gates. The VHDL code is organized into modules. The code would be implemented on the BASYS3 at the end of the lab.

**Methodology:**

Initially, eight different functions were determined for the three-bit system. First, a half adder was made. Then a full adder was created using this half adder. Eight different functions were designed using these two components or logic gates. At the end of each design, the design was checked and visualized by creating the RLT schematic. The waveform was created with a testbench, and the design was verified. The constraint file is created, and the bitstream is generated. Finally, the design was simulated with switches and LEDs on BASYS3.

## Design Specifications:


In the ALU, there are 7 inputs and 1 output. First, the desired function is selected with the selection(m) switches in the three-bit system. Then, x1, x2, x3 and y1, y2, y3 three-bit numbers are determined by switches. The four-bit output is projected via LEDs.

The VHDL code is organized into modules. The top-level module, "top.vhdl" outputs the outcomes of the specified operation and toggles between user options.

There are ten sub-modules under the top module:

- ❖ halfadder.vhdl
- ❖ fulladder.vhdl
- ❖ addition.vhdl
- ❖ subtraction.vhdl
- ❖ comparator.vhdl
- ❖ left\_logical\_shifter.vhdl
- ❖ ones\_complement.vhdl
- ❖ andgate.vhdl
- ❖ norgate.vhdl
- ❖ xnorgate.vhdl

BASYS3 FPGA was programmed via a constraints file for implementation according to the following assignments:

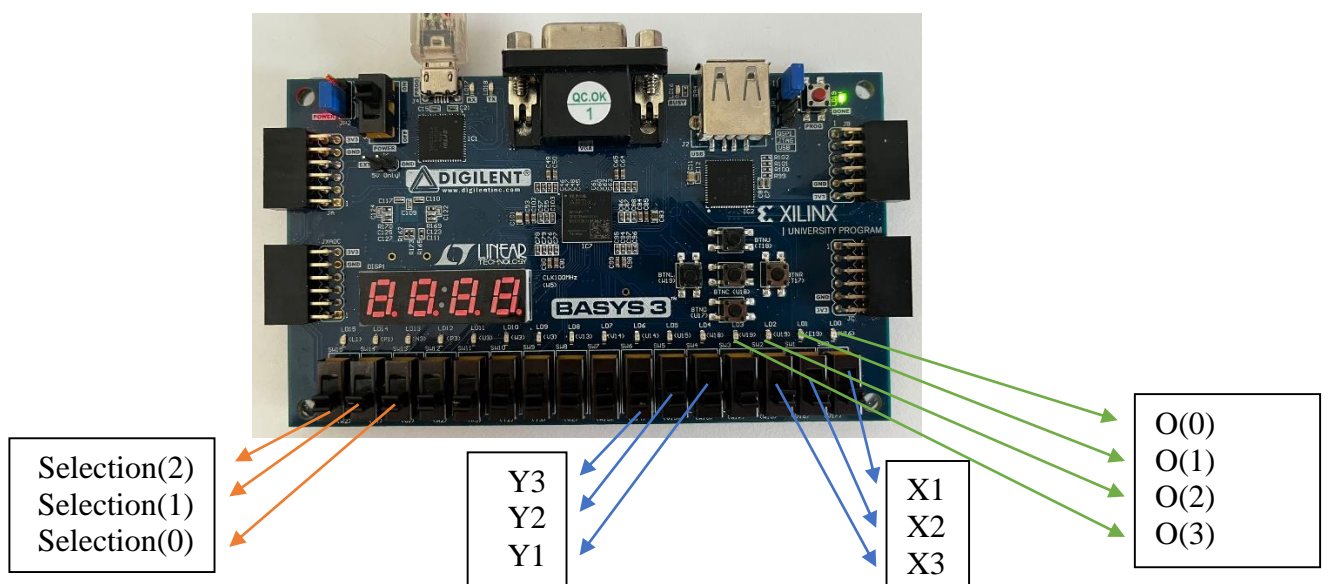Table 1: Input and Output Assignments

## Results:

The testbench was written for simulation, and the waveform was created with three different input pairs (“111” and “111”, “111” and “000”, “101” and “010”). Verified that all functions work correctly when the results are checked, as seen in Figure B.

 


Figure ii: The Waveform of ALU

Comparing the expected output with the output on the FPGA after entering random inputs into each function to verify that the implementation is working correctly.

### i. ADDITION

Selection: “000”

Input 1: “100”

Input 2: “111”

Expected: “1011”

 


Figure i addition


## ii. SUBTRACTION

Selection: "001"

Input 1: "010"

Input 2: "101"

Expected: "0101"

 

*Figure ii subtraction*


## iii. COMPARATOR

Selection: "010"

Input 1: "111"

Input 2: "111"

Expected: "0100"

 


*Figure iii comparator*

## iv. LEFT\_LOGICAL\_SHIFT

Selection: "011"

Input 2: "101"

Expected: "0010"

 

*Figure iv left logic shift*

## v. ONES\_COMPLEMENT

Selection: "100"

Input 2: "111"

Expected: "0000"

## vi. AND\_GATE

Selection: "101"

Input 1: "111"

Input 2: "110"

Expected: "0110"

## vii. NOR\_GATE

Selection: "110"

Input 1: "000"

Input 2: "000"

Expected: "0111"


## viii. XNOR\_GATE

Selection: "111"


Input 1: "001"

Input 2: "011"


Expected: "0101"

 


*Figure v ones complement*

 

*Figure vi and gate*

 

*Figure vii nor gate*

 

*Figure viii xnor gate*

## **Conclusion:**

Using VHDL and Basys3, an Arithmetic Logic Unit was constructed in this lab. Three 3-bit variables are inputted into the design, and eight different functions are used to generate a 4-bit output. The VHDL code is organized into modules. The half adder made with logic gates was used to construct the full adder. So how to use a function as a module within another function was learned. Then eight different functions were designed using these two sub-modules or logic gates. The designs were checked with the help of RTL schematics and waveforms. Finally, the design was implemented on the FPGA. The outputs are compared with the simulation's waveform and the equation's expected results so the design is verified. No errors were encountered in this lab, except for human errors that occurred during circuit design. These errors were fixed by schematizing and simulating with the Vivado. Thanks to all this, it was learned to build ALU and use modules/sub-modules.

## Appendix:

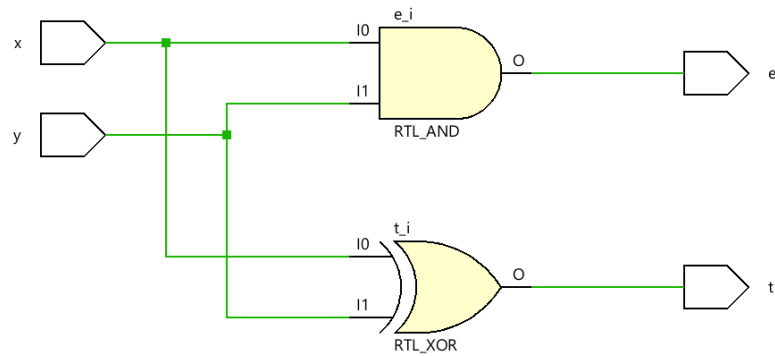


Figure iii: Half Adder Schematic

 


Figure iv: Full Adder Schematic

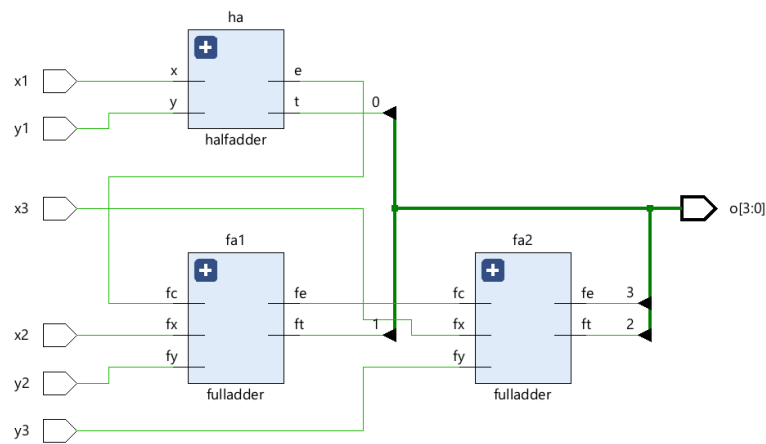


Figure v: Addition Schematic



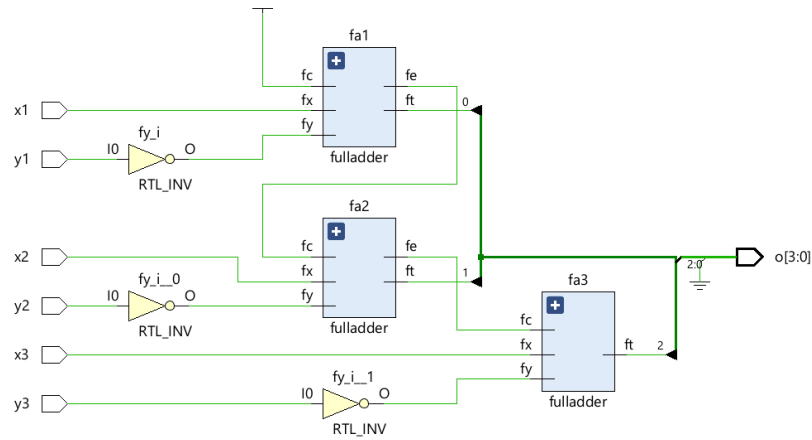


Figure vi: Subtraction Schematic

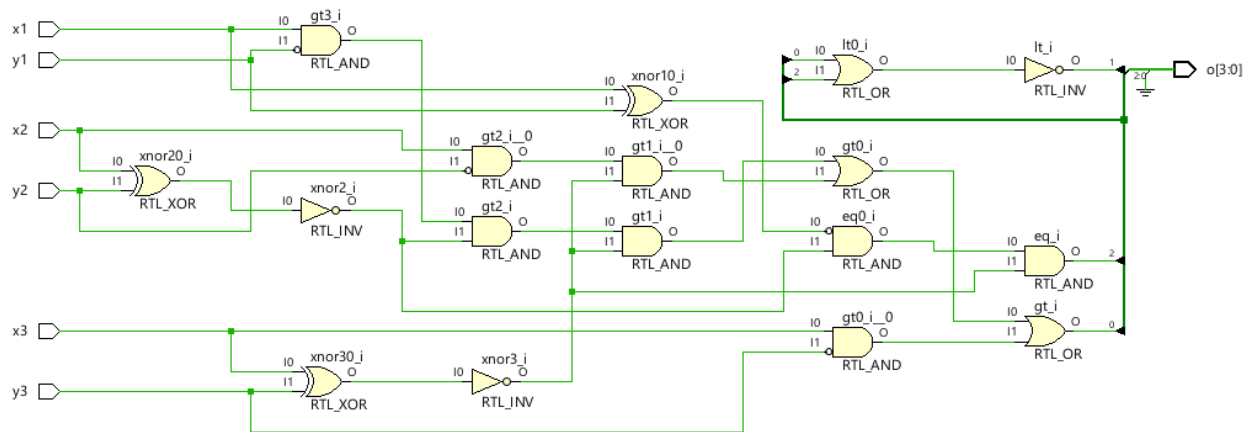


Figure vii: Comparator Schematic

 


Figure viii: Left Logical Shift Schematic

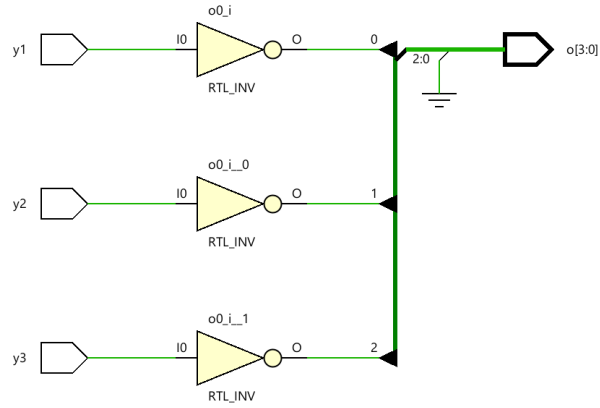


Figure ix: One's Complement Schematic

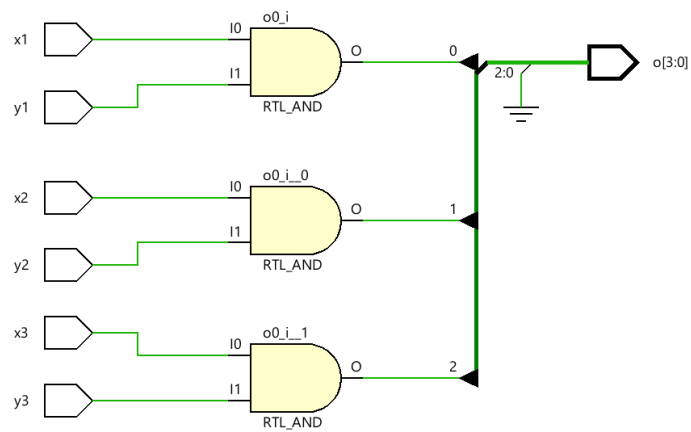


Figure x: AND Gate Schematic

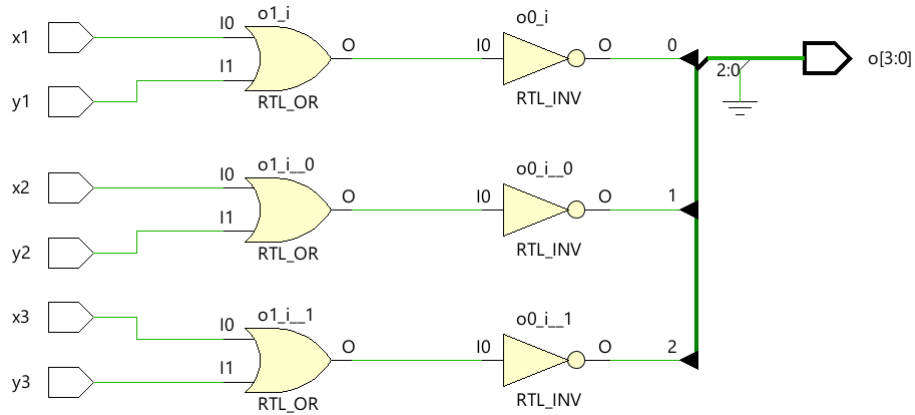


Figure xi: NOR Gate Schematic

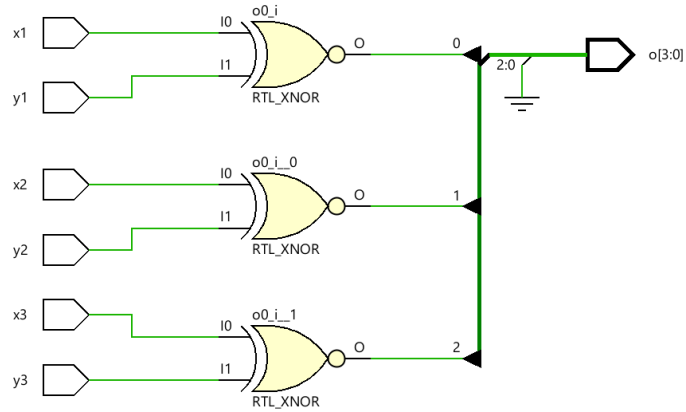


Figure xii: XNOR Gate Schematic

## TOP

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity top is
```

```
    Port ( x1, x2, x3, y1, y2, y3 : in STD_LOGIC;
```

```
          selection : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          o : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end top;
```

```
architecture Behavioral of top is
```

```
    component addition
```

```
        Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
              o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
    end component;
```

```
    component subtraction
```

```
        Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
              o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
    end component;
```

```
    component comparator
```

```
        Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
              o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
component left_logical_shift
```

```
Port ( x1, x2, x3: in STD_LOGIC;
```

```
o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
component ones_complement
```

```
Port ( y1, y2, y3: in STD_LOGIC;
```

```
o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
component and_gate
```

```
Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
component nor_gate
```

```
Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
component xnor_gate
```

```
Port ( x1, x2, x3, y1, y2,y3 : in STD_LOGIC;
```

```
o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end component;
```

```
signal inp_a1, inp_a2, inp_a3, inp_b1, inp_b2, inp_b3: std_logic;
```

```
signal o1, o2, o3, o4, o5, o6, o7, o8: std_logic_vector(3 downto 0);
```

```
begin
```

```
inp_a1 <= x1;
```

```
inp_a2 <= x2;
```

```
inp_a3 <= x3;
```

```
inp_b1 <= y1;
```

```
inp_b2 <= y2;
```

```
inp_b3 <= y3;
```

```
function1: addition
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o1);
```

```
function2: subtraction
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o2);
```

```
function3: comparator
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o3);
```

```
function4: left_logical_shift
```

```
port map(x1 => inp_b1, x2 => inp_b2, x3 => inp_b3,  
         o => o4);
```

```
function5: ones_complement
```

```
port map(y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o5);
```

```
function6: and_gate
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o6);
```

```
function7: nor_gate
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o7);
```

```
function8: xnor_gate
```

```
port map(x1 => inp_a1, x2 => inp_a2, x3 => inp_a3,  
         y1 => inp_b1, y2 => inp_b2, y3 => inp_b3,  
         o => o8);
```

```
process(selection, o1, o2, o3, o4, o5, o6, o7, o8)
```

```
begin
```

```

if selection = "000" then

    o <= o1;

elsif selection = "001" then

    o <= o2;

elsif selection = "010" then

    o <= o3;

elsif selection = "011" then

    o <= o4;

elsif selection = "100" then

    o <= o5;

elsif selection = "101" then

    o <= o6;

elsif selection = "110" then

    o <= o7;

elsif selection = "111" then

    o <= o8;

else

    o <= "0000";

end if;

end process;

end Behavioral;

```

## HALFADDER

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

entity halfadder is

```

    Port ( x,y : in STD_LOGIC;

           e,t : out STD_LOGIC);

end halfadder;

```

architecture Behavioral of halfadder is

```

begin

e <= x and y;

t <= x xor y;

```

```
end Behavioral;
```

## **FULLADDER**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fulladder is
```

```
    port ( fx,fy,fc : in STD_LOGIC;
```

```
           fe,ft : out STD_LOGIC);
```

```
end fulladder;
```

```
architecture Behavioral of fulladder is
```

```
    signal ht1,he1,he2: std_logic;
```

```
    component halfadder
```

```
        port ( x,y : in STD_LOGIC;
```

```
               e,t : out STD_LOGIC);
```

```
    end component;
```

```
    begin
```

```
    ha1: halfadder
```

```
        port map(fx,fy,he1,ht1);
```

```
    ha2: halfadder
```

```
        port map(fc,ht1,he2,ft);
```

```
    fe <= he1 or he2;
```

```
end Behavioral;
```

## **ADDITION**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity addition is
```

```
    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;
```

```
           o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end addition;
```

```
architecture Behavioral of addition is
```

```
signal he,fa1e :std_logic;
```

```
component halfadder
```

```
    port ( x,y : in STD_LOGIC;
```

```
           e,t : out STD_LOGIC);
```

```
end component;
```

```
component fulladder
```

```
    port ( fx,fy,fc : in STD_LOGIC;
```

```
           fe,ft : out STD_LOGIC);
```

```
end component;
```

```
begin
```

```
ha: halfadder
```

```
    port map(x1,y1,he,o(0));
```

```
fa1: fulladder
```

```
    port map(x2,y2,he,fa1e,o(1));
```

```
fa2: fulladder
```

```
    port map(x3,y3,fa1e,o(3),o(2));
```

```
end Behavioral;
```

## SUBTRACTION

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity subtraction is
```

```
    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;
```

```
           o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end subtraction;
```

```
architecture Behavioral of subtraction is
```

```
signal fa1e,fa2e,ignore :std_logic;
```

```
component fulladder
```

```
    port ( fx,fy,fc : in STD_LOGIC;
```

```
           fe,ft : out STD_LOGIC);
```

```
end component;
```



```

begin

fa1: fulladder

    port map(x1,not y1,'1',fa1e,o(0));

fa2: fulladder

    port map(x2,not y2,fa1e,fa2e,o(1));

fa3: fulladder

    port map(x3,not y3,fa2e,ignore,o(2));

o(3) <= '0';

end Behavioral;

```

## COMPARATOR

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity comparator is

    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;

          o : out STD_LOGIC_VECTOR(3 downto 0));

end comparator;

```

architecture Behavioral of comparator is

```

signal xnor1, xnor2, xnor3, gt, eq, lt: std_logic;

begin

xnor1 <= not (x1 xor y1);

xnor2 <= not (x2 xor y2);

xnor3 <= not (x3 xor y3);

gt <= (x1 and ( not y1) and xnor2 and xnor3) or (x2 and (not y2) and xnor3) or (x3 and (not y3));

eq <= xnor1 and xnor2 and xnor3;

lt <= not (gt or eq);

o(0) <= gt;

o(1) <= lt;

o(2) <= eq;

o(3) <= '0';

end Behavioral;

```

## LEFT\_LOGICAL\_SHIFT

```

library IEEE;

```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity left_logical_shift is
```

```
    Port ( x1,x2,x3 : in STD_LOGIC;
```

```
          o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end left_logical_shift;
```

```
architecture Behavioral of left_logical_shift is
```

```
begin
```

```
o(0) <= '0';
```

```
o(1) <= x3;
```

```
o(2) <= x2;
```

```
o(3) <= '0';
```

```
end Behavioral;
```

## ONES\_COMPLEMENT

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity ones_complement is
```

```
    Port ( y1,y2,y3 : in STD_LOGIC;
```

```
          o : out STD_LOGIC_VECTOR(3 downto 0));
```

```
end ones_complement;
```

```
architecture Behavioral of ones_complement is
```

```
begin
```

```
o(0) <= not y1;
```

```
o(1) <= not y2;
```

```
o(2) <= not y3;
```

```
o(3) <= '0';
```

```
end Behavioral;
```

## AND\_GATE

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity and_gate is

    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;

           o : out STD_LOGIC_VECTOR(3 downto 0));

end and_gate;

```

architecture Behavioral of and\_gate is

```

begin

o(0) <= x1 and y1;

o(1) <= x2 and y2;

o(2) <= x3 and y3;

o(3) <= '0';

end Behavioral;

```

## NOR\_GATE

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity nor_gate is

    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;

           o : out STD_LOGIC_VECTOR(3 downto 0));

end nor_gate;

```

architecture Behavioral of nor\_gate is

```

begin

o(0) <= x1 nor y1;

o(1) <= x2 nor y2;

o(2) <= x3 nor y3;

o(3) <= '0';

end Behavioral;

```

## XNOR\_GATE

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity xnor_gate is

    Port ( x1,x2,x3,y1,y2,y3 : in STD_LOGIC;

           o : out STD_LOGIC_VECTOR(3 downto 0));

end xnor_gate;

```

```

architecture Behavioral of xnor_gate is

```

```

begin

o(0) <= x1 xnor y1;

o(1) <= x2 xnor y2;

o(2) <= x3 xnor y3;

o(3) <= '0';

end Behavioral;

```

## TEST\_TOP

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity test_top is

-- Port ( );

end test_top;

architecture Behavioral of test_top is

component top

    Port ( x1, x2, x3, y1, y2, y3 : in STD_LOGIC;

           selection : in STD_LOGIC_VECTOR (2 downto 0);

           o : out STD_LOGIC_VECTOR (3 downto 0));

end component;

signal x1, x2, x3, y1, y2, y3 : std_logic;

signal selection: std_logic_vector(2 downto 0);

signal o: std_logic_vector(3 downto 0);

begin

func: top

```

```
port map(x1,x2,x3,y1,y2,y3, selection,o);
```

```
test_top: process
```

```
begin
```

```
    selection <= "000";
```

```
    x1 <= '0';
```

```
    x2 <= '0';
```

```
    x3 <= '0';
```

```
    y1 <= '0';
```

```
    y2 <= '0';
```

```
    y3 <= '0';
```

```
wait for 25ns;
```

```
    selection <= "000";
```

```
    x1 <= '1';
```

```
    x2 <= '1';
```

```
    x3 <= '1';
```

```
    y1 <= '1';
```

```
    y2 <= '1';
```

```
    y3 <= '1';
```

```
wait for 25ns;
```

```
    selection <= "001";
```

```
    x1 <= '1';
```

```
    x2 <= '1';
```

```
    x3 <= '1';
```

```
    y1 <= '1';
```

```
    y2 <= '1';
```

```
    y3 <= '1';
```

```
wait for 25ns;
```

```
    selection <= "010";
```

```
    x1 <= '1';
```

```
    x2 <= '1';
```

```
    x3 <= '1';
```

```
    y1 <= '1';
```

```
    y2 <= '1';
```

```
    y3 <= '1';
```

```
wait for 25ns;
```

```
selection <= "011";

x1 <= '1';

x2 <= '1';

x3 <= '1';

y1 <= '1';

y2 <= '1';

y3 <= '1';

wait for 25ns;

selection <= "100";

x1 <= '1';

x2 <= '1';

x3 <= '1';

y1 <= '1';

y2 <= '1';

y3 <= '1';

wait for 25ns;

selection <= "101";

x1 <= '1';

x2 <= '1';

x3 <= '1';

y1 <= '1';

y2 <= '1';

y3 <= '1';

wait for 25ns;

selection <= "110";

x1 <= '1';

x2 <= '1';

x3 <= '1';

y1 <= '1';

y2 <= '1';

y3 <= '1';

wait for 25ns;

selection <= "111";

x1 <= '1';

x2 <= '1';
```

```
x3 <= '1';  
y1 <= '1';  
y2 <= '1';  
y3 <= '1';  
wait for 25ns;  
selection <= "000";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "001";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "010";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "011";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';
```

```
y3 <= '0';  
wait for 25ns;  
selection <= "100";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "101";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "110";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "111";  
x1 <= '1';  
x2 <= '1';  
x3 <= '1';  
y1 <= '0';  
y2 <= '0';  
y3 <= '0';  
wait for 25ns;  
selection <= "000";
```



```
x1 <= '1';
x2 <= '0';
x3 <= '1';
y1 <= '0';
y2 <= '1';
y3 <= '0';
wait for 25ns;

selection <= "001";

x1 <= '1';
x2 <= '0';
x3 <= '1';
y1 <= '0';
y2 <= '1';
y3 <= '0';
wait for 25ns;

selection <= "010";

x1 <= '1';
x2 <= '0';
x3 <= '1';
y1 <= '0';
y2 <= '1';
y3 <= '0';
wait for 25ns;

selection <= "011";

x1 <= '1';
x2 <= '0';
x3 <= '1';
y1 <= '0';
y2 <= '1';
y3 <= '0';
wait for 25ns;

selection <= "100";

x1 <= '1';
x2 <= '0';
x3 <= '1';
```

```
y1 <= '0';
y2 <= '1';
y3 <= '0';
wait for 25ns;

selection <= "101";

x1 <= '1';
x2 <= '0';
x3 <= '1';

y1 <= '0';
y2 <= '1';
y3 <= '0';

wait for 25ns;

selection <= "110";

x1 <= '1';
x2 <= '0';
x3 <= '1';

y1 <= '0';
y2 <= '1';
y3 <= '0';

wait for 25ns;

selection <= "111";

x1 <= '1';
x2 <= '0';
x3 <= '1';

y1 <= '0';
y2 <= '1';
y3 <= '0';

end process;

end Behavioral;
```